

ORIGIN := 1

$$C := (0.990732 \quad 0.55772 \quad 0.124707)^T \quad K := 2$$

$$\omega_0 := 2 \cdot \pi \cdot 100 = 628.319 \quad \text{частота среза}$$

неравномерность в дБ $\epsilon = 1$

$$B := (0.124362 \quad 0.339763 \quad 0.464125)^T$$

$$\omega_1 := 750$$

$$W_1(p) := \frac{K \cdot C_1 \cdot \omega_0^2}{p^2 + B_1 \cdot p \cdot \omega_0 + C_1 \cdot \omega_0^2}$$

$$W_2(p) := \frac{K \cdot C_2 \cdot \omega_0^2}{p^2 + B_2 \cdot p \cdot \omega_0 + C_2 \cdot \omega_0^2}$$







$$W_3(p) := \frac{K \cdot C_3 \cdot \omega_0^2}{p^2 + B_3 \cdot p \cdot \omega_0 + C_3 \cdot \omega_0^2}$$

$$z := (9i \quad 9i + \omega_0 \quad 8i + \omega_0 \quad 8i \quad 0 \quad \omega_0 \quad 8i + \omega_0)^T$$

$$z_1 := (\omega_1 \quad \omega_1 + j \quad i + \omega_0 \cdot 10)^T$$

$$\omega_0 = 628.319$$
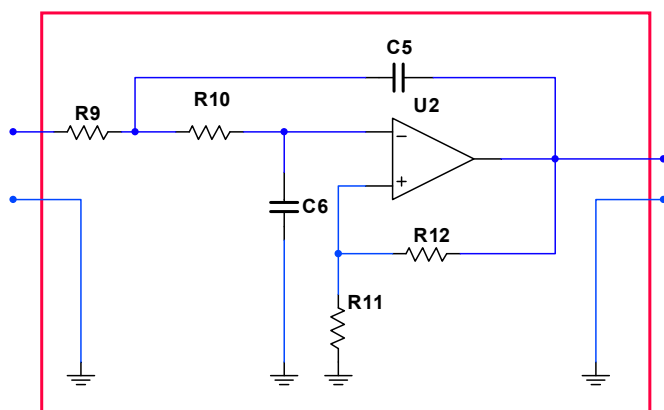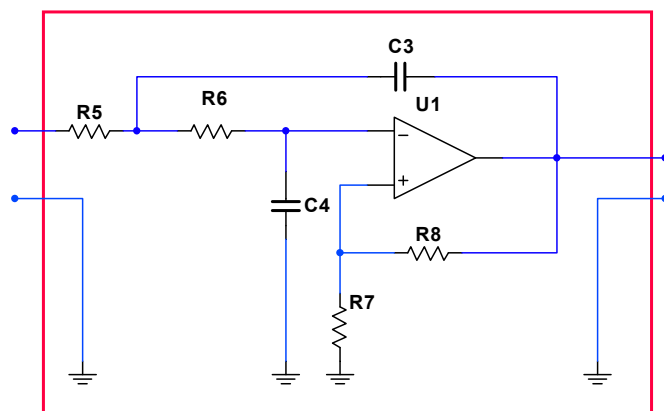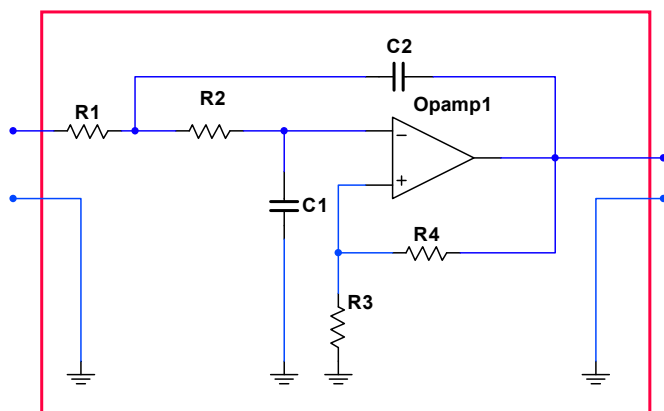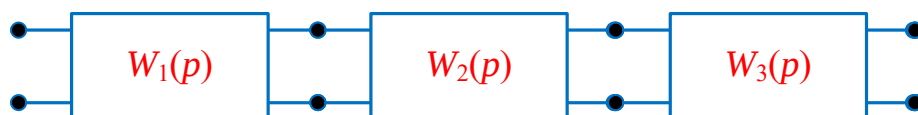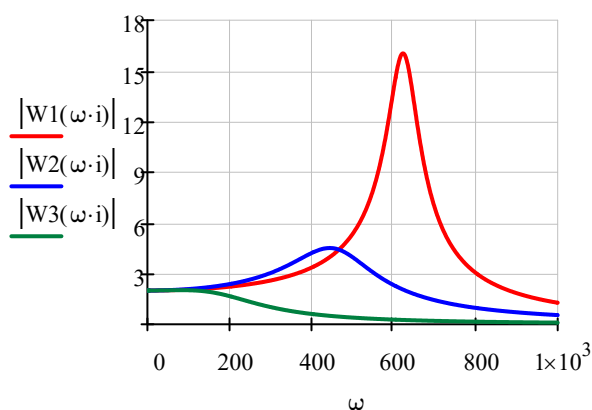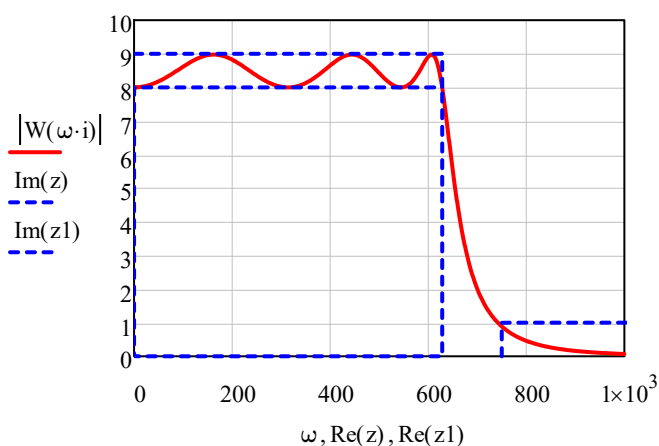
$$W(p) := W_1(p) \cdot W_2(p) \cdot W_3(p) \quad \omega := 0, 1 \dots 10^3$$



Расчет первого звена

$$C_2 := 0.1 \cdot 10^{-6} \quad C := C_1 \quad B := B_1$$

$$C_1 := \frac{[B^2 + 4 \cdot C \cdot (K - 1)] \cdot C_2}{4 \cdot C} \quad C_1 = 1.004 \times 10^{-7} \quad \text{Начинаем расчет с радикала (корень квадратный)}$$

$$R_1 := \frac{2}{[B \cdot C_1 + \sqrt{[B^2 + 4 \cdot C \cdot (K - 1)] \cdot C_2^2 - 4 \cdot C \cdot C_1 \cdot C_2}] \cdot \omega_0} \quad R_1 = 2.54959 \times 10^5$$

$$R_2 := \frac{1}{\omega_0^2 \cdot C \cdot C_1 \cdot C_2 \cdot R_1} \quad R_2 = 998.899$$

$$R_3 := \frac{K \cdot (R_1 + R_2)}{K - 1} \quad R_3 = 5.119 \times 10^5$$

$$R_4 := K \cdot (R_1 + R_2) \quad R_4 = 5.119 \times 10^5$$

$$\underline{H1(p)} := \frac{K \cdot C_0 \cdot \omega_0^2}{p^2 + B_0 \cdot p \cdot \omega_0 + C_0 \cdot \omega_0^2} \quad \underline{K} := 1 + \frac{R_3}{R_4} \quad C \cdot \omega_0^2 = 3.911 \times 10^5$$


$$K = 2 \quad \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2} = 3.911 \times 10^5$$

$$B \cdot \omega_0 = 78.139$$

$$\frac{1}{C_2} \cdot \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{1}{R_2 \cdot C_1} \cdot \left(\frac{R_3}{R_4} \right) = 78.14$$

$$\underline{H1(p)} := \frac{\left(1 + \frac{R_3}{R_4} \right) \cdot \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}{p^2 + \left[\frac{1}{C_2} \cdot \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{1}{R_2 \cdot C_1} \cdot \left(\frac{R_3}{R_4} \right) \right] \cdot p + \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}$$

$$\omega := 0, 1 \dots 10^3$$

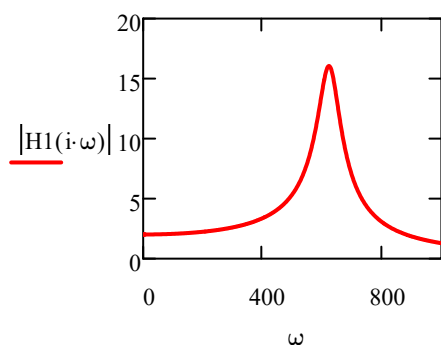

Расчет второго звена

$$\underline{C_2} := 0.1 \cdot 10^{-6} \quad \underline{C} := C_2 \quad \underline{B} := B_2$$

$$C_1 := \frac{[B^2 + 4 \cdot C \cdot (K - 1)] \cdot C_2}{4 \cdot C} \quad C_1 = 1.052 \times 10^{-7}$$

$$R_1 := \frac{2}{[B \cdot C_1 + \sqrt{[B^2 + 4 \cdot C \cdot (K - 1)] \cdot C_2^2 - 4 \cdot C \cdot C_1 \cdot C_2}] \cdot \omega_0} \quad R_1 = 89076.51478$$

$$R_2 := \frac{1}{\omega_0^2 \cdot C \cdot C_1 \cdot C_2 \cdot R_1} \quad R_2 = 4.848 \times 10^3$$

$$R_3 := \frac{K \cdot (R_1 + R_2)}{K - 1} \quad R_3 = 1.878 \times 10^5$$

$$R_4 := K \cdot (R_1 + R_2) \quad R_4 = 1.878 \times 10^5$$

$$H2(p) := \frac{K \cdot C \cdot \omega_0^2}{p^2 + B \cdot p \cdot \omega_0 + C \cdot \omega_0^2} \quad K := 1 + \frac{R_3}{R_4} \quad C \cdot \omega_0^2 = 2.202 \times 10^5$$


$$K = 2 \quad \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2} = 2.202 \times 10^5$$

$$B \cdot \omega_0 = 213.479$$

$$\frac{1}{C_2} \cdot \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{1}{R_2 \cdot C_1} \cdot \left(\frac{R_3}{R_4} \right) = 213.751$$

$$H2(p) := \frac{\left(1 + \frac{R_3}{R_4} \right) \cdot \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}{p^2 + \left[\frac{1}{C_2} \cdot \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{1}{R_2 \cdot C_1} \cdot \left(\frac{R_3}{R_4} \right) \right] \cdot p + \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}$$

$$\omega := 0, 1 \dots 10^3$$

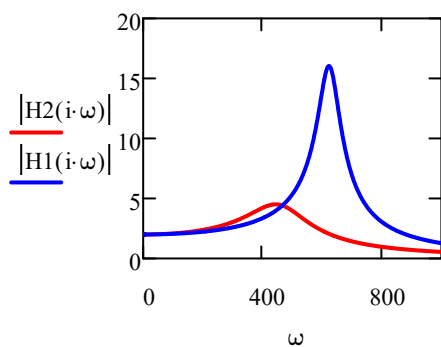

Расчет третьего звена

$$C_2 := 0.1 \cdot 10^{-6} \quad C := C_3 \quad B := B_3$$

$$C_1 := \frac{[B^2 + 4 \cdot C \cdot (K - 1)] \cdot C_2}{4 \cdot C} \quad C_1 = 1.432 \times 10^{-7}$$

$$R_1 := \frac{2}{[B \cdot C_1 + \sqrt{[B^2 + 4 \cdot C \cdot (K - 1)] \cdot C_2^2 - 4 \cdot C \cdot C_1 \cdot C_2}] \cdot \omega_0} \quad R_1 = 47898.48863$$

$$R_2 := \frac{1}{\omega_0^2 \cdot C \cdot C_1 \cdot C_2 \cdot R_1} \quad R_2 = 2.962 \times 10^4$$

$$\underline{\underline{R_3}} := \frac{K \cdot (R_1 + R_2)}{K - 1} \qquad R_3 = 1.55 \times 10^5$$

$$\underline{\underline{R_4}} := K \cdot (R_1 + R_2) \qquad R_4 = 1.55 \times 10^5$$

$$H3(p) := \frac{K \cdot C \cdot \omega_o^2}{p^2 + B \cdot p \cdot \omega_o + C \cdot \omega_o^2} \qquad \underline{\underline{K}} := 1 + \frac{R_3}{R_4} \qquad C \cdot \omega_o^2 = 4.923 \times 10^4$$


$$K = 2 \qquad \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2} = 4.923 \times 10^4$$

$$B \cdot \omega_o = 291.618$$

$$\frac{1}{C_2} \cdot \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{1}{R_2 \cdot C_1} \cdot \left(\frac{R_3}{R_4} \right) = 310.609$$

$$\underline{\underline{H3(p)}} := \frac{\left(1 + \frac{R_3}{R_4} \right) \cdot \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}{p^2 + \left[\frac{1}{C_2} \cdot \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{1}{R_2 \cdot C_1} \cdot \left(\frac{R_3}{R_4} \right) \right] \cdot p + \frac{1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}$$

$$\omega := 0,1 \dots 10^3$$

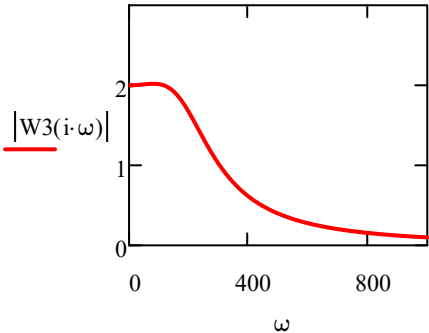

$$\underline{\underline{A(\omega)}} := H1(\omega) \cdot H2(\omega) \cdot H3(\omega)$$

