
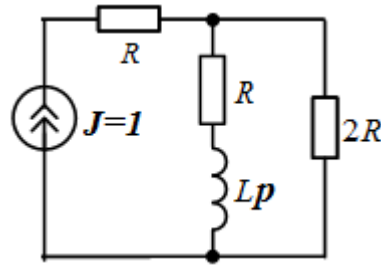


Найти ток индуктивности

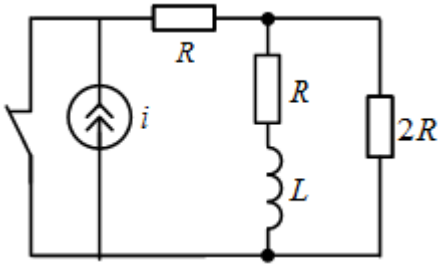

$$J := 1$$

$$L := 0.1 \quad R := 10$$

$$I(p) := \frac{2 \cdot R}{3 \cdot R + L \cdot p}$$

$$I(p) = \frac{2 \cdot R}{3 \cdot R} \cdot \left(\frac{1}{1 + p \cdot \frac{L}{3 \cdot R}} \right)$$



$$w(t) := \frac{2 \cdot R}{L} \cdot e^{\frac{-3 \cdot R}{L} \cdot t}$$

$$\tau := \frac{L}{R \cdot 3} = 3.333 \times 10^{-3}$$


$$i(t) := \int_0^t w(t - \tau) d\tau$$

$$\frac{2 \cdot R}{L} = 200$$
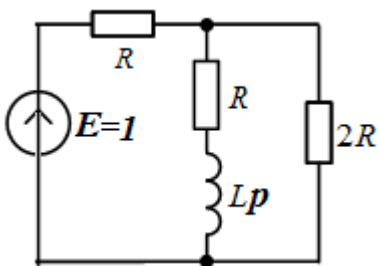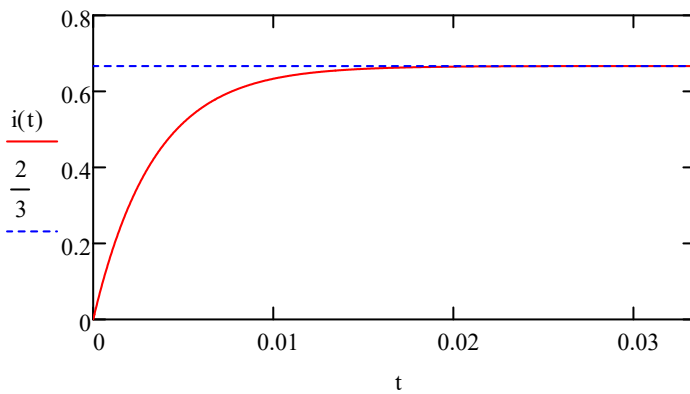
$$t := 0, 0.01 \cdot \tau .. 10 \cdot \tau$$



$$E := 1$$

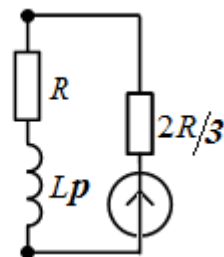

$$W(p) := \frac{E \cdot 2}{3} \cdot \frac{1}{\left(R + \frac{2}{3} \cdot R + L \cdot p \right)}$$

$$w(t) := \frac{E \cdot 2}{3 \cdot L} \cdot e^{\frac{-R \cdot 5}{L \cdot 3} \cdot t}$$

$$w(t) := \frac{E \cdot 2}{3 \cdot L} \cdot e^{-\frac{R \cdot 5}{L \cdot 3} \cdot t}$$

$$\tau := \frac{L \cdot 3}{R \cdot 5} = 6 \times 10^{-3}$$

$$i(t) := \int_0^t w(t - \tau) d\tau$$

$$\frac{2 \cdot R}{L} = 200$$

$$t := 0, 0.01 \cdot \tau .. 10 \cdot \tau$$

