



Boolean Algebra


Logic Gates

Introduction

- Hardware consists of a few simple building blocks
 - These are called *logic gates*
 - AND, OR, NOT, ...
 - NAND, NOR, XOR, ...
- Logic gates are built using transistors
 - NOT gate can be implemented by a single transistor
 - AND gate requires 3 transistors
- Transistors are the fundamental devices
 - Pentium processor consists of 3 million transistors
 - Now we can build chips with more than 100 million transistors

Basic Concepts

 - Simple gates
 - AND
 - OR
 - NOT
- Functionality can be expressed by a truth table
 - A truth table lists output for each possible input combination
- Precedence
 - NOT > AND > OR
 - $F = A \bar{B} + \bar{A} B$
 $= (A (\bar{B})) + ((\bar{A}) B)$



AND gate

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1



OR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1



NOT gate


A	F
0	1
1	0

Logic symbol

Truth table

Basic Concepts (cont.)

 - Additional useful gates
 - NAND
 - NOR
 - XOR
- $\text{NAND} = \text{AND} + \text{NOT}$
- $\text{NOR} = \text{OR} + \text{NOT}$
- XOR implements exclusive-OR function
- NAND and NOR gates require only 2 transistors
 - AND and OR need 3 transistors!



NAND gate

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0



NOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



XOR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Logic symbol

Truth table

Basic Concepts (cont.)


- Number of functions
 - With N logical variables, we can define 2^{2^N} functions
 - Some of them are useful
 - AND, NAND, NOR, XOR, ...
 - Some are not useful:
 - Output is always 1
 - Output is always 0
 - “Number of functions” definition is useful in proving completeness property

Basic Concepts (cont.)


- Complete sets
 - A set of gates is complete
 - If we can implement any logical function using only the type of gates in the set
 - You can use as many gates as you want
 - Some example complete sets
 - {AND, OR, NOT} ← Not a minimal complete set
 - {AND, NOT}
 - {OR, NOT}
 - {NAND}
 - {NOR}
 - Minimal complete set
 - A complete set with no redundant elements.

Basic Concepts (cont.)


- Proving NAND gate is universal

 

AND gate

 


NOT gate

 


OR gate

Basic Concepts (cont.)


- Proving NOR gate is universal

 

OR gate

 


NOT gate

 


AND gate


Logic Chips

 


7408

 

7432

 

7486

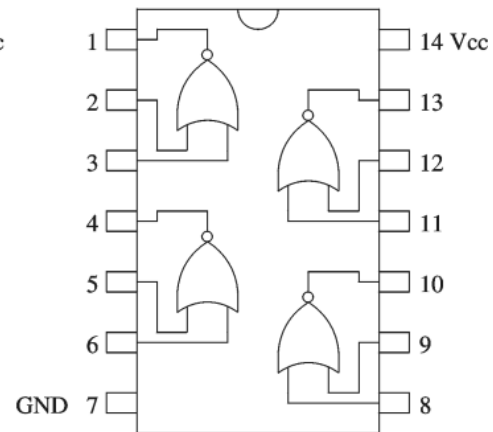

7402

Logic Chips (cont.)

- Integration levels
 - SSI (small scale integration)
 - Introduced in late 1960s
 - 1-10 gates (previous examples)
 - MSI (medium scale integration)
 - Introduced in late 1960s
 - 10-100 gates
 - LSI (large scale integration)
 - Introduced in early 1970s
 - 100-10,000 gates
 - VLSI (very large scale integration)
 - Introduced in late 1970s
 - More than 10,000 gates

Logic Functions

- Logical functions can be expressed in several ways:
 - Truth table
 - Logical expressions
 - Graphical form
- Example:
 - Majority function
 - Output is one whenever majority of inputs is 1
 - We use 3-input majority function


Logic Functions (cont.)

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


- Logical expression form

$$F = A B + B C + A C$$

 


Logical Equivalence

 
- All three circuits implement $F = A B$ function



(a)

 

(b)

 


(c)

Logical Equivalence (cont.)

- Proving logical equivalence of two circuits
 - Derive the logical expression for the output of each circuit
 - Show that these two expressions are equivalent
 - Two ways:
 - You can use the truth table method
 - » For every combination of inputs, if both expressions yield the same output, they are equivalent
 - » Good for logical expressions with small number of variables
 - You can also use algebraic manipulation
 - » Need Boolean identities

Logical Equivalence (cont.)

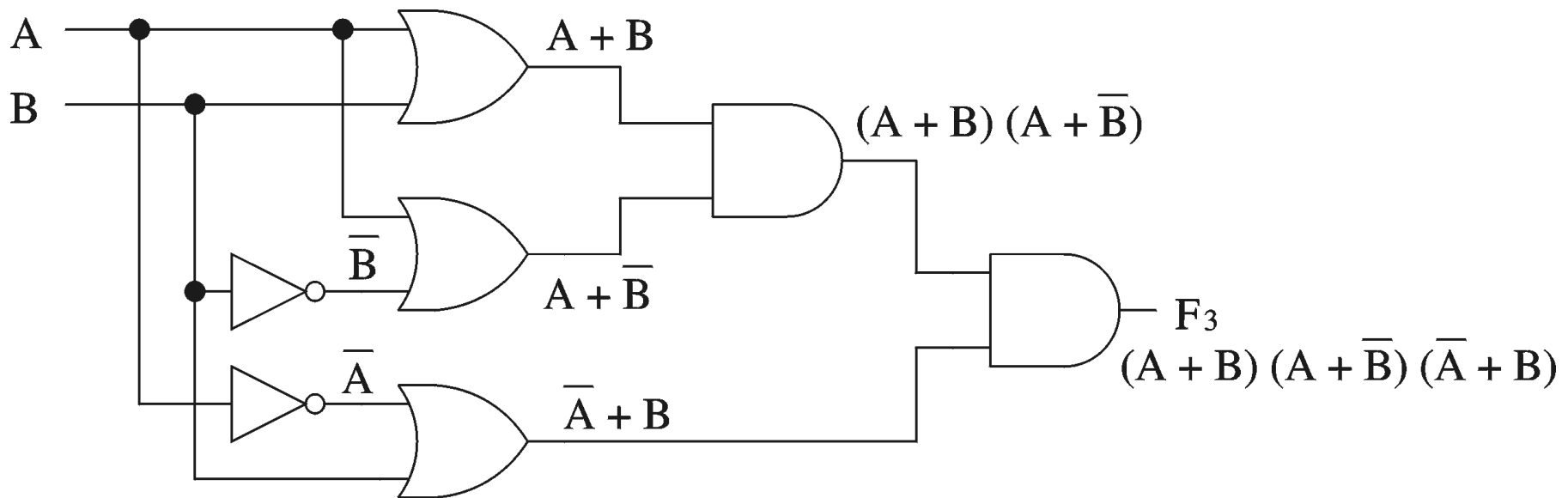- Derivation of logical expression from a circuit
 - Trace from the input to output
 - Write down intermediate logical expressions along the path



Logical Equivalence (cont.)

- Proving logical equivalence: Truth table method

A	B	F1 = A B	F3 = (A + B) (A + \bar{B}) (\bar{A} + B)
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

Boolean Algebra

Boolean identities

Name	AND version	OR version
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y + z) = xy + xz$	$x + (y \cdot z) =$ $(x + y) (x + z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$

Boolean Algebra (cont.)


Name	AND version	OR version
Involution	$\overline{\overline{x}} = x$	---
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) =$
de Morgan	$\overline{x \cdot y} = \overline{x} + \overline{y}$	$(x + y) + z$ $\overline{x + y} = \overline{x} \cdot \overline{y}$

Boolean Algebra (cont.)

- Proving logical equivalence: Boolean algebra method
 - To prove that two logical functions $F1$ and $F2$ are equivalent
 - Start with one function and apply Boolean laws to derive the other function
 - Needs intuition as to which laws should be applied and when
 - Practice helps!
 - Sometimes it may be convenient to reduce both functions to the same expression
 - Example: $F1 = A B$ and $F3$ are equivalent

Logic Circuit Design Process

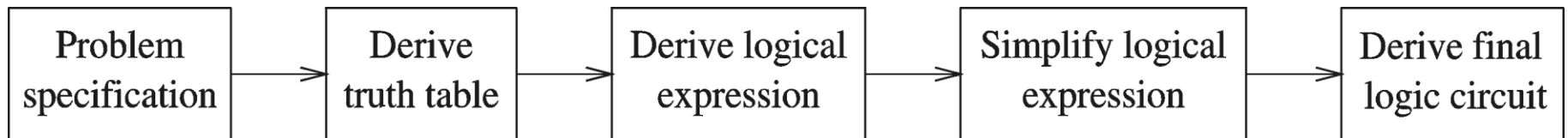- A simple logic design process involves
 - Problem specification
 - Truth table derivation
 - Derivation of logical expression
 - Simplification of logical expression
 - Implementation



Deriving Logical Expressions

- Derivation of logical expressions from truth tables
 - sum-of-products (SOP) form
 - product-of-sums (POS) form
- SOP form
 - Write an AND term for each input combination that produces a 1 output
 - Write the variable if its value is 1; complement otherwise
 - OR the AND terms to get the final expression
- POS form
 - Dual of the SOP form

Deriving Logical Expressions

- 3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- SOP logical expression
- Four product terms
 - Because there are 4 rows with a 1 output

$$F = \overline{A} B \overline{C} + A \overline{B} C + A B \overline{C} + A B C$$

Deriving Logical Expressions

- 3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- POS logical expression

- Four sum terms

– Because there are 4 rows with a 0 output

$$F = (A + B + C) (A + \overline{B} + C) (\overline{A} + B + C) (\overline{A} + \overline{B} + C)$$

Logical Expression Simplification

– Algebraic manipulation

- Use Boolean laws to simplify the expression
 - Difficult to use
 - Don't know if you have the simplified form

Algebraic Manipulation

- Majority function example

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC =$$

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC + \overbrace{ABC + ABC}^{\text{Added extra}}$$

- We can now simplify this expression as

$$BC + AC + AB$$

- A difficult method to use for complex expressions

Implementation Using NAND Gates

- Using NAND gates
 - Get an equivalent expression

$$A B + C D = \overline{\overline{A B + C D}}$$

- Using de Morgan's law

$$A B + C D = \overline{\overline{A B} \cdot \overline{C D}}$$


- Can be generalized
 - Majority function

$$A B + B C + A C = \overline{\overline{A B} \cdot \overline{B C} \cdot \overline{A C}}$$

Idea: NAND Gates: Sum-of-Products, NOR Gates: Product-of-Sums

Implementation Using NAND Gates (cont.)

- Majority function

 

Introduction to Combinational Circuits

- Combinational circuits
 - Output depends only on the current inputs
- Combinational circuits provide a higher level of abstraction
 - Help in reducing design complexity
 - Reduce chip count
- We look at some useful combinational circuits