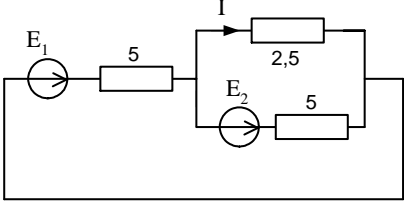
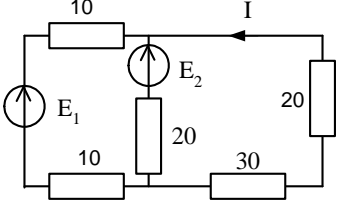
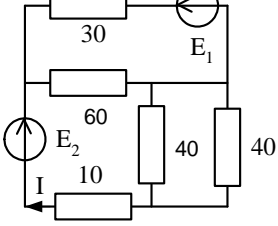
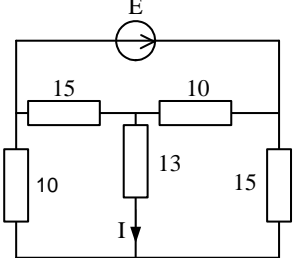
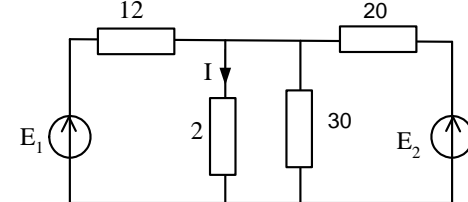
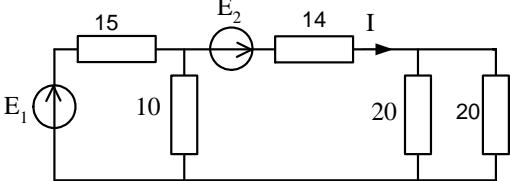



## Assignment

1. Find current  $I$  by the following methods:








- Mesh Current Method;
- Node Voltage Method;
- Thévenin Equivalent Method.







№ of variant	Network parameters	Equivalent circuit
1	Given: $E_1=100$ (V); $E_2=60$ (V); $R$ in $\Omega$ (Ohms). Find: $I$ -?	
2	Given: $E_1=100$ (V); $E_2=20$ (V); $R$ in $\Omega$ (Ohms). Find: $I$ -?	
3	Given: $E_1=90$ (V); $E_2=160$ (V); $R$ in $\Omega$ (Ohms). Find: $I$ -?	
4	Given: $E=50$ (V); $R$ in $\Omega$ (Ohms). Find: $I$ -?	
5	Given: $E_1=100$ (V); $E_2=60$ (V); $R$ in $\Omega$ (Ohms). Find: $I$ -?	
6	Given: $E_1=26$ (V); $E_2=6$ (V); $R$ in $\Omega$ (Ohms). Find: $I$ -?	

7	<p>Given:  <math>E_1=120</math> (V); <math>E_2=20</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).            Find: <math>I</math> -?</p>	
8	<p>Given:  <math>E=100</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).            Find: <math>I</math> -?</p>	
9	<p>Given:  <math>E_1=100</math> (V); <math>E_2= E_3=20</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).            Find: <math>I</math> -?</p>	
10	<p>Given:  <math>E_1=50</math> (V); <math>E_2=20</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).            Find: <math>I</math> -?</p>	
11	<p>Given:  <math>E_1=20</math> (V); <math>E_2=50</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).            Find: <math>I</math> -?</p>	
12	<p>Given:  <math>E_1=80</math> (V); <math>E_2=40</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).            Find: <math>I</math> -?</p>	
13	<p>Given:  <math>E_1=50</math> (V); <math>E_2=30</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).            Find: <math>I</math> -?</p>	

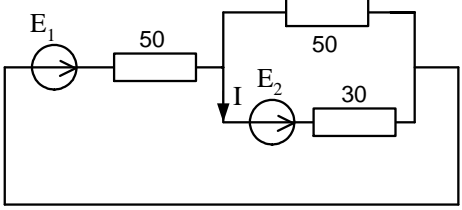14	<p>Given:  <math>E_1=10</math> (V); <math>E_2=6</math> (V);  <math>R</math> in <math>\Omega</math> (Ohms).          Find: <math>I</math> -?</p>	
----	---	--

2. Find current  $i(t)$  or voltage  $u(t)$  by the Classical Method to Transient Analysis:

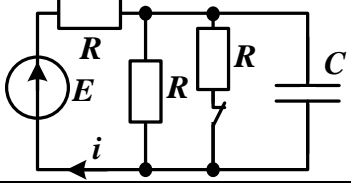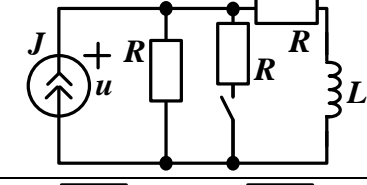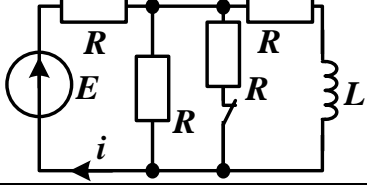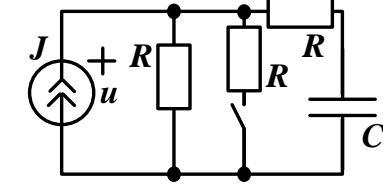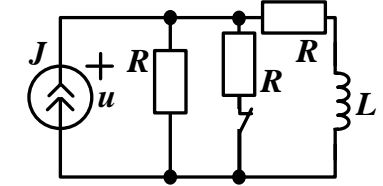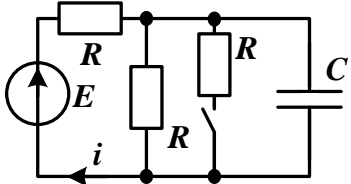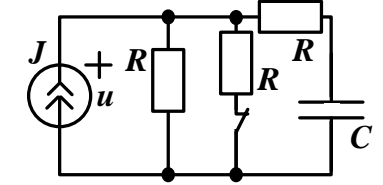№ of variant	Network parameters	Equivalent circuit
1	<p>Given:  <math>E=80</math> (V); <math>C=100</math> (<math>\mu</math>F);  <math>R=50</math> (<math>\Omega</math>).          Find: <math>i(t)</math>-?</p>	
2	<p>Given:  <math>J=1</math> (A); <math>L=100</math> (mH);  <math>R=100</math> (<math>\Omega</math>).          Find: <math>u_j(t)</math>-?</p>	
3	<p>Given:  <math>E=150</math> (V); <math>L=50</math> (mH);  <math>R=50</math> (<math>\Omega</math>).          Find: <math>i(t)</math>-?</p>	
4	<p>Given:  <math>J=2</math> (A); <math>C=100</math> (<math>\mu</math>F);  <math>R=50</math> (<math>\Omega</math>).          Find: <math>u_j(t)</math>-?</p>	
5	<p>Given:  <math>J=5</math> (A); <math>L=150</math> (mH);  <math>R=150</math> (<math>\Omega</math>).          Find: <math>u_j(t)</math>-?</p>	
6	<p>Given:  <math>E=50</math> (V); <math>C=100</math> (<math>\mu</math>F);  <math>R=50</math> (<math>\Omega</math>).          Find: <math>i(t)</math>-?</p>	
7	<p>Given:  <math>J=3</math> (A); <math>C=120</math> (<math>\mu</math>F);  <math>R=120</math> (<math>\Omega</math>).          Find: <math>u_j(t)</math>-?</p>	

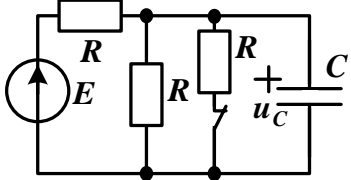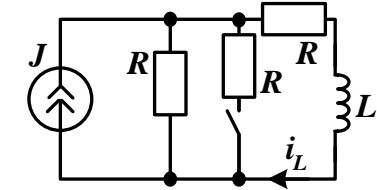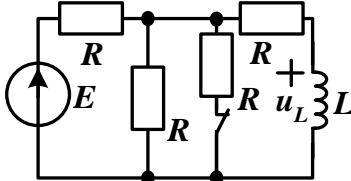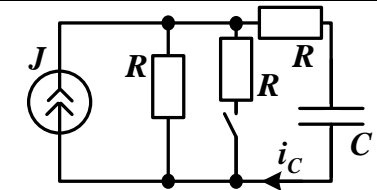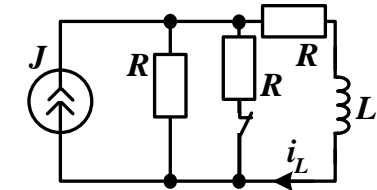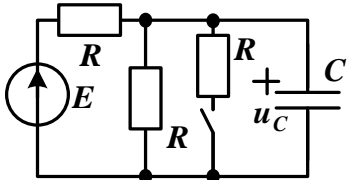8	<p>Given:  <math>E=120</math> (V); <math>C=80</math> (<math>\mu\text{F}</math>);  <math>R=90</math> (<math>\Omega</math>).            Find: <math>u_C(t)</math>-?</p>	
9	<p>Given:  <math>J=4</math> (A); <math>L=40</math> (mH);  <math>R=20</math> (<math>\Omega</math>).            Find: <math>i_L(t)</math>-?</p>	
10	<p>Given:  <math>E=160</math> (V); <math>L=40</math> (mH);  <math>R=60</math> (<math>\Omega</math>).            Find: <math>u_L(t)</math>-?</p>	
11	<p>Given:  <math>J=1</math> (A); <math>C=100</math> (<math>\mu\text{F}</math>);  <math>R=50</math> (<math>\Omega</math>).            Find: <math>i_C(t)</math>-?</p>	
12	<p>Given:  <math>J=2</math> (A); <math>L=40</math> (mH);  <math>R=70</math> (<math>\Omega</math>).            Find: <math>i_L(t)</math>-?</p>	
13	<p>Given:  <math>E=110</math> (V); <math>C=80</math> (<math>\mu\text{F}</math>);  <math>R=70</math> (<math>\Omega</math>).            Find: <math>u_C(t)</math>-?</p>	
14	<p>Given:  <math>J=3</math> (A); <math>C=80</math> (<math>\mu\text{F}</math>);  <math>R=50</math> (<math>\Omega</math>).            Find: <math>i_R(t)</math>-?</p>	